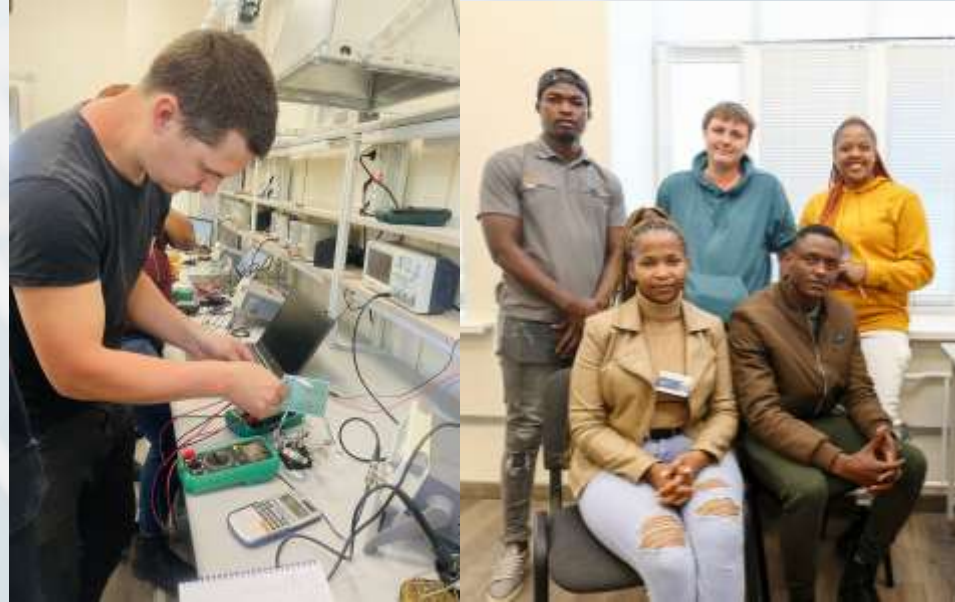


# Electronics & RF hands-on training

## Compiled by:

- Athenkosi Siyalo, University of Western Cape
- Tafadzwa Mabate, University of Johannesburg
- Emmanuel Kgoedi, University of Limpopo
- Lungile Hadebe, University of KwaZulu Natal

Laboratory: University center



Supervised by: Dmitriy Belozarov (electronics)  
Kirill Verlamov (Rf technology)



# Introduction

## Microwave RF radiation



Radionavigation



Accelerator technics



Portable electronics




Home appliances

RF



Space television

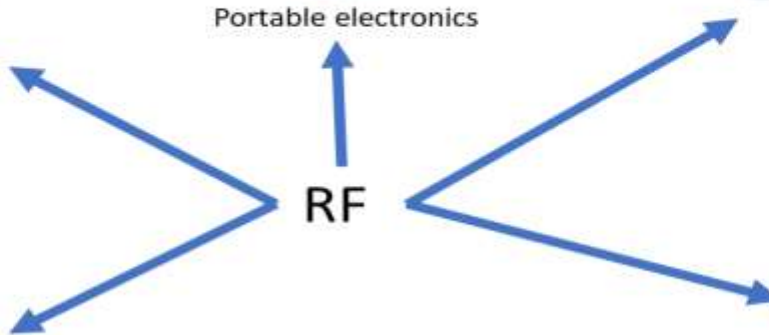

# Introduction cont'd



Oscilloscope



RF Generator



VNA




Diaphragms



Oscilloscope probe



Soldering iron

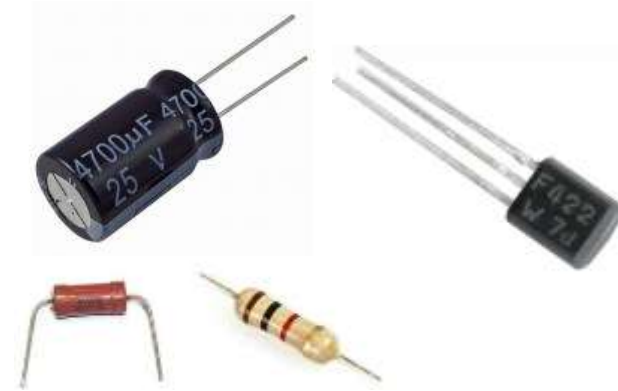

Resistors, capacitor and transistor <sup>3</sup>

# Aims

- Explore the application of fundamental radioelectronic components, ability to interpret electronic circuits, and grasp the fundamental principles behind electronic devices
- Provide an overview of the key elements of RF technology and demonstrating how waves behave under different conditions.
  - scenarios without any obstacles as well as situations involving various heterogeneity



# Objectives

- Basics of Rf technology
- Determining the wavelength in the waveguide
- Matching quality coefficients (SWR, TWR and  $\rho_h$ )
- Determining total resistance of different irregularities theoretically and practically




# Objectives

- Utilize the reactive dowel for narrow band matching
- Develop skills in calculating the cavity quality factor
- Soldering basic skills
- Evaluating the properties of semiconductors
- Calculation of stage transistor amplifiers



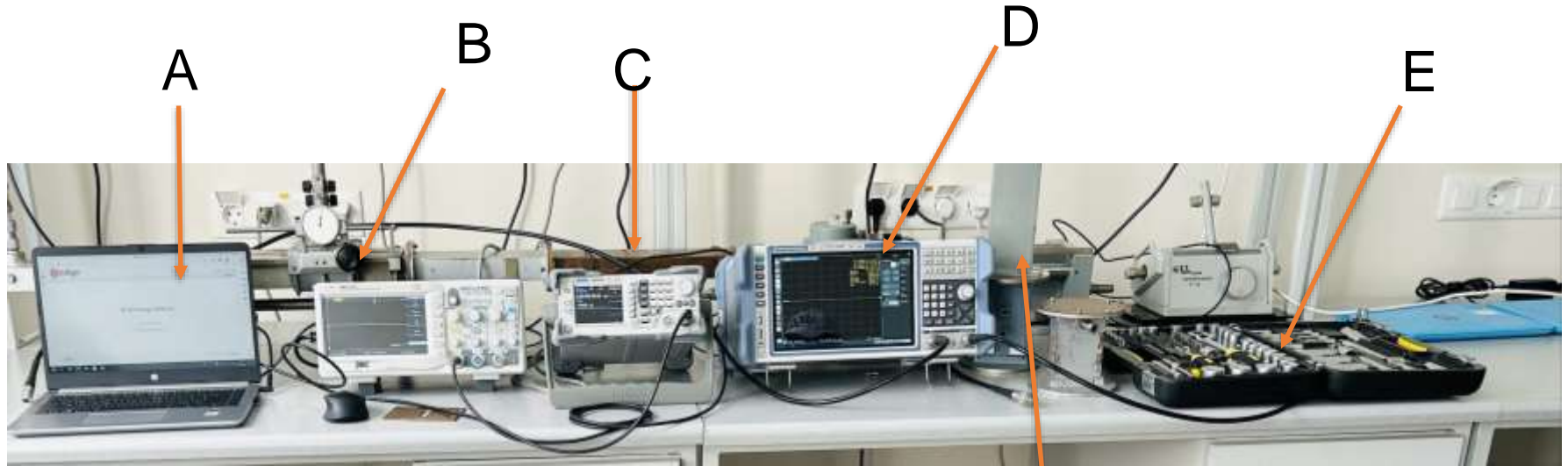
# Experiment Procedure:RF Technology

Instruments: oscilloscope, a RF generator, vector network analyzer



# Results and discussion: Determining wavelength

RF Power transmission	Wavelength (cm)	
	Coaxial line ( $\lambda_w$ )	10.50
Planar line ( $\lambda_w$ )	10.50	10.86
Waveguide ( $\lambda_w$ )	15.34	15.30

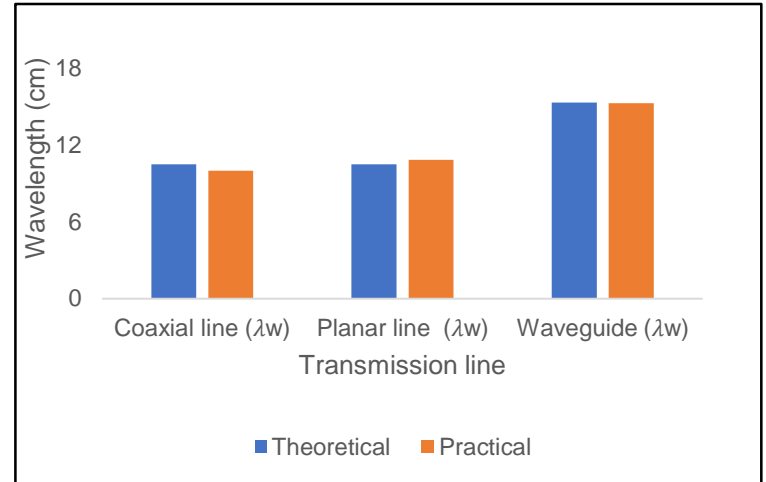

$$\lambda_w = \frac{\lambda_o}{\sqrt{\epsilon}}$$

$$\lambda_w = \frac{\lambda_o}{\sqrt{1 - \frac{\lambda_o^2}{\lambda_{cr}^2 \epsilon \mu} \sqrt{\epsilon \mu}}}$$





## Results and discussion: Matching quality coefficients

Setup	Z min (cm)	Z max (cm)	U min (mV)	U max (mV)	SWR ( $\frac{U_{max}}{U_{min}}$ )
ML	12,9	13.3	173	175	1,01
OW	8.00	11.4	100	200	2.00
ID	4.00	8.40	10.0	32.0	3,20
CD	4.00	6.00	4.00	15.0	3,75
Cal	35.0	10.3	0.00	350	$\infty$



# Results and discussion: Total resistance (Theoretically)

$$Z = R + jX$$




$$Y = \frac{1}{Z}$$



$$Z_L^* = \frac{2SWR - j(1 - SWR^2) \sin \varphi}{(SWR^2 + 1) - (SWR^2 - 1) \cos \varphi}$$

$$\varphi = \frac{4\pi\Delta z}{\lambda_W}$$
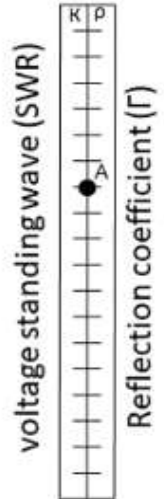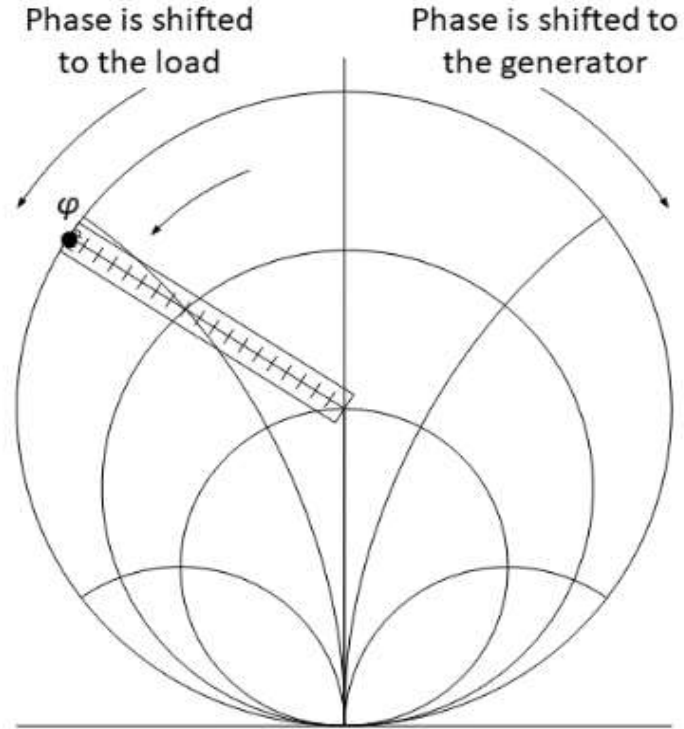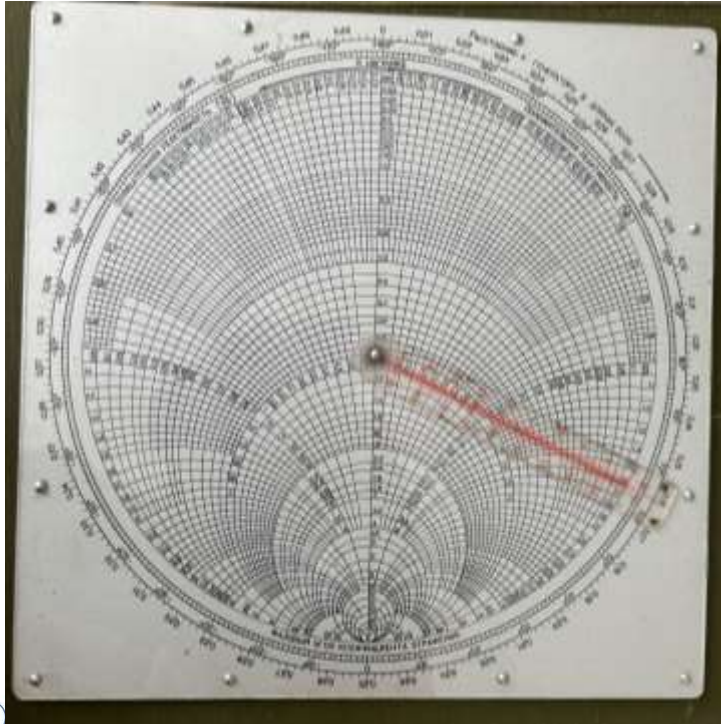
# Results and discussion: Total resistance (Smith Chart)



# Results and discussion: Total resistance



# Results and discussion: total resistance

Setup	Angle ( $\varphi$ )	SWR	Z (theoretical)	Z (VNA)
ML	1.35	1.01	$1.00 + j0.01$	$0.92 + j1.25$
OW	5.37	2.00	$1.26 + j0.75$	$0.62 + j0.50$
ID	8.64	3.20	$0.36 - j0.37$	$0.36 - j0.42$
CD	8.64	3.75	$0.31 + j0.38$	$0.31 + j0.42$
S	16.8	$\infty$	-	-




# Results and discussion: Reactive dowel

Height (mm)	$\varphi$	SWR	Z	Y (theoretical)	Y (practical)
0	6.5	1.86	$1.75 + j6.5$	0.00	-0.14
2	6.3	1.97	$1.79 + j4.2$	-0.51	-0.20
4	5.8	1.81	$1.29 + j2.1$	-0.29	-0.35
6	6.1	1.91	$1.50 + j3.0$	-0.13	-0.27
8	6.0	1.76	$1.48 + j2.6$	-0.13	-0.29
10	5.9	1.79	$1.38 + j2.4$	-0.00008	-0.32







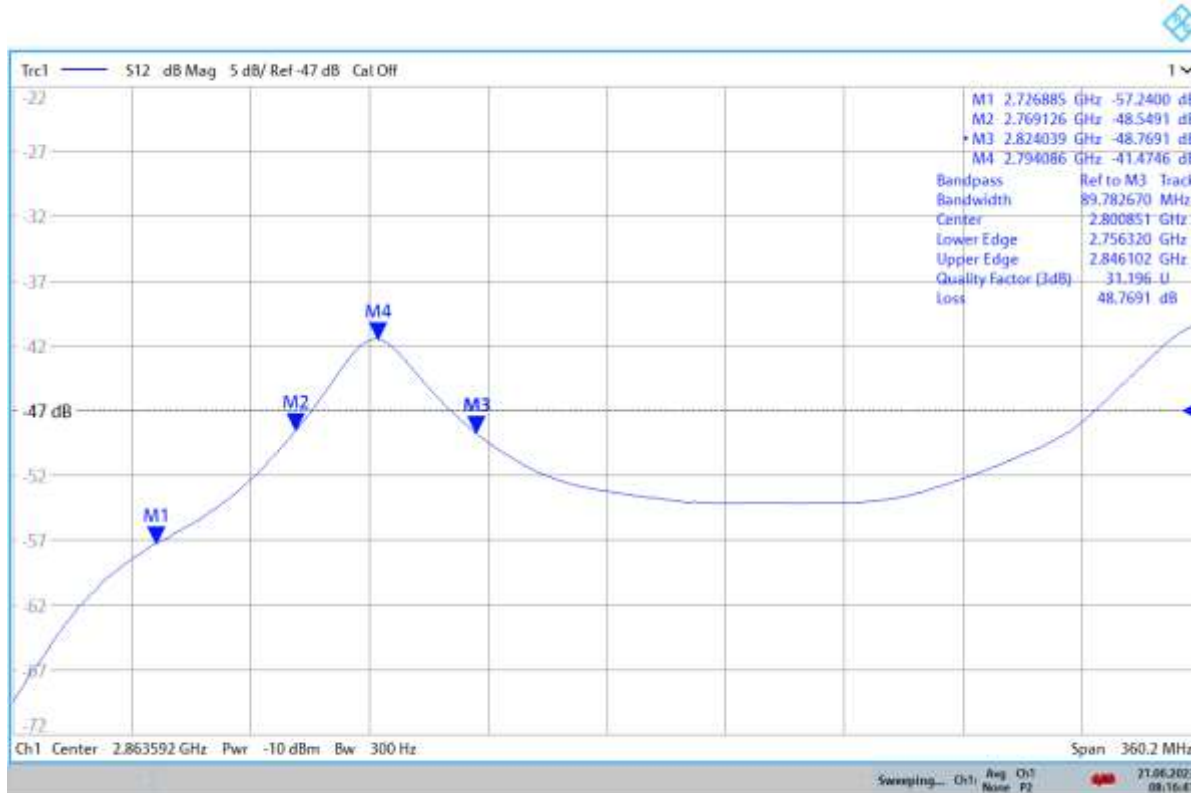
# Results and discussion: cavity resonator



08:16:42 21.06.2023





# Voltage divider and RC circuit

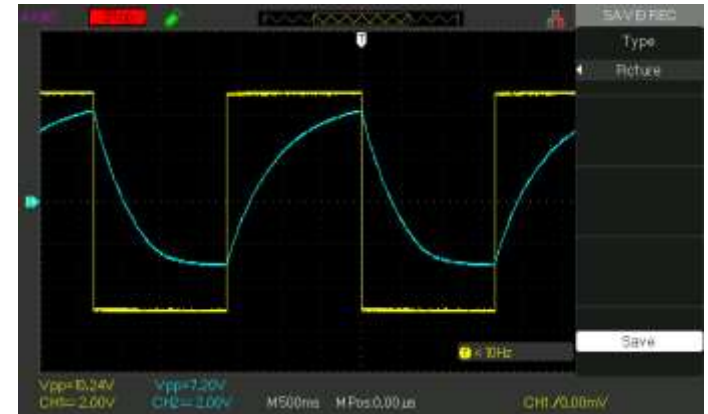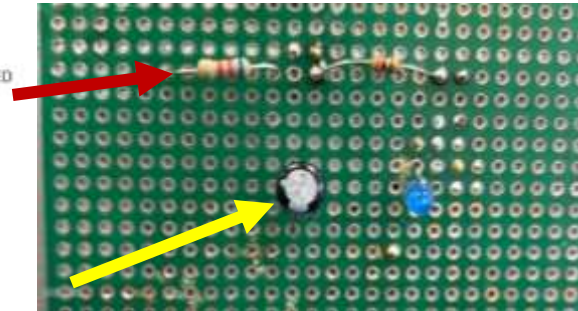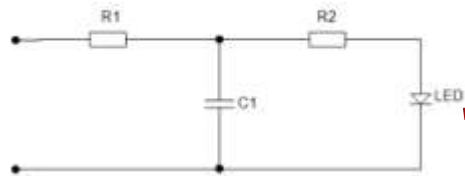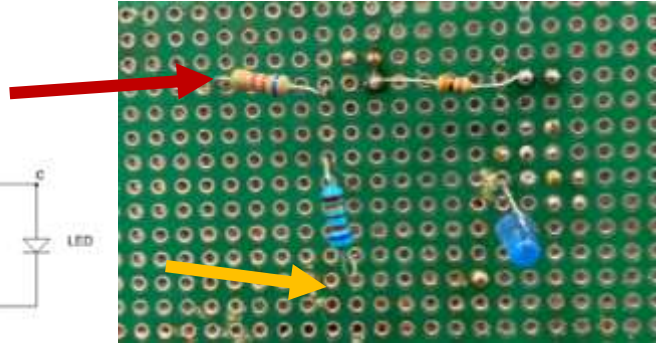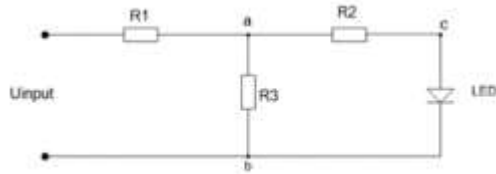








# Reverse and forward diode connection

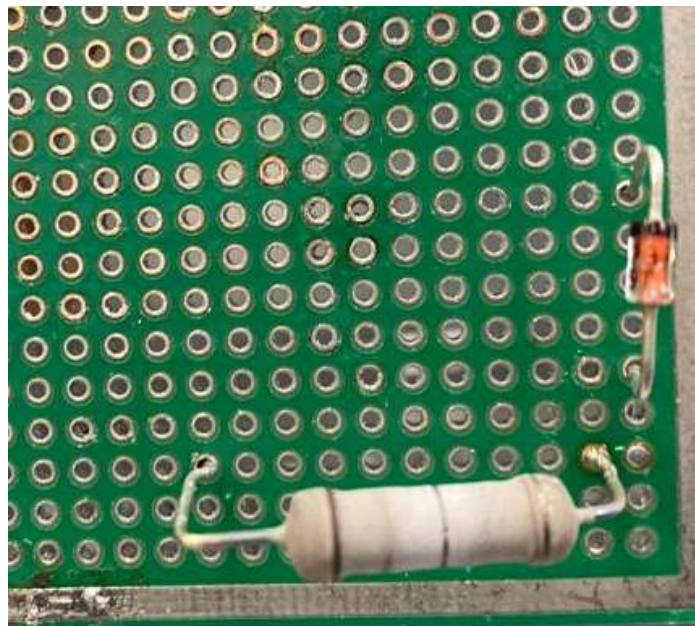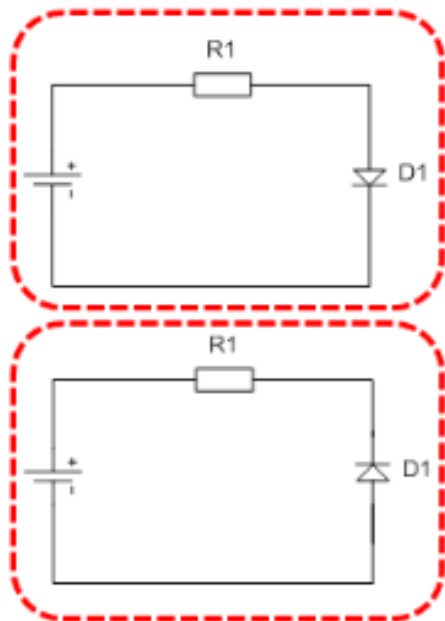

# Characteristic V(A) of the diode

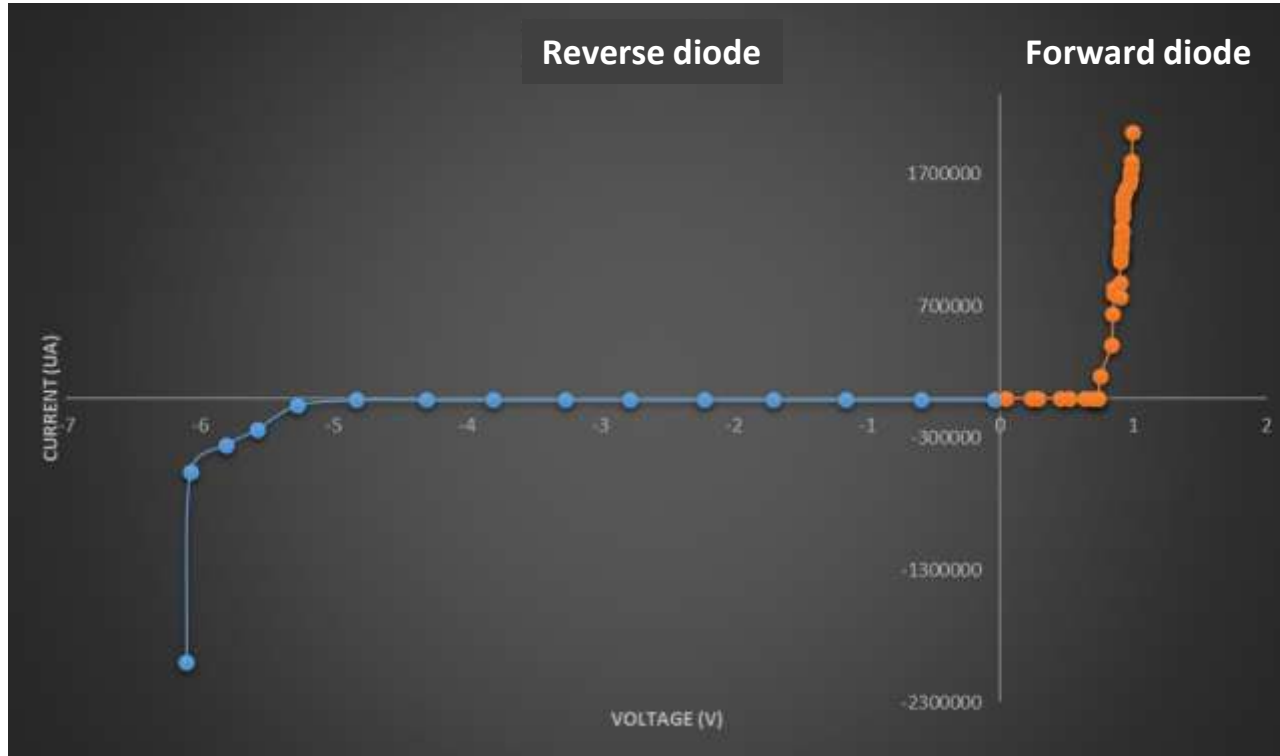

# Diode application

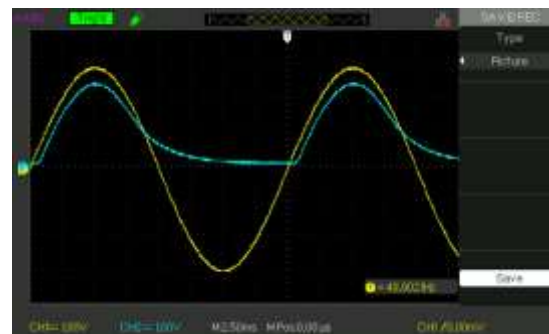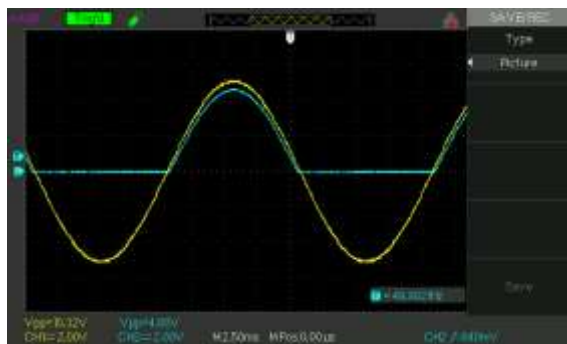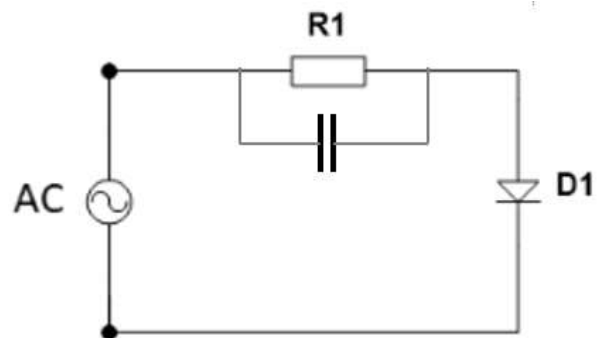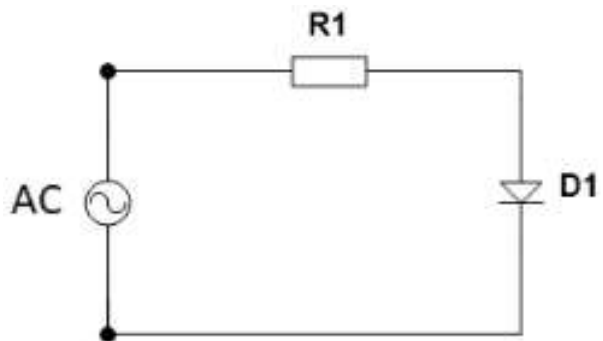


1 $\mu$ F




# Diode application cont'd



3.3uF

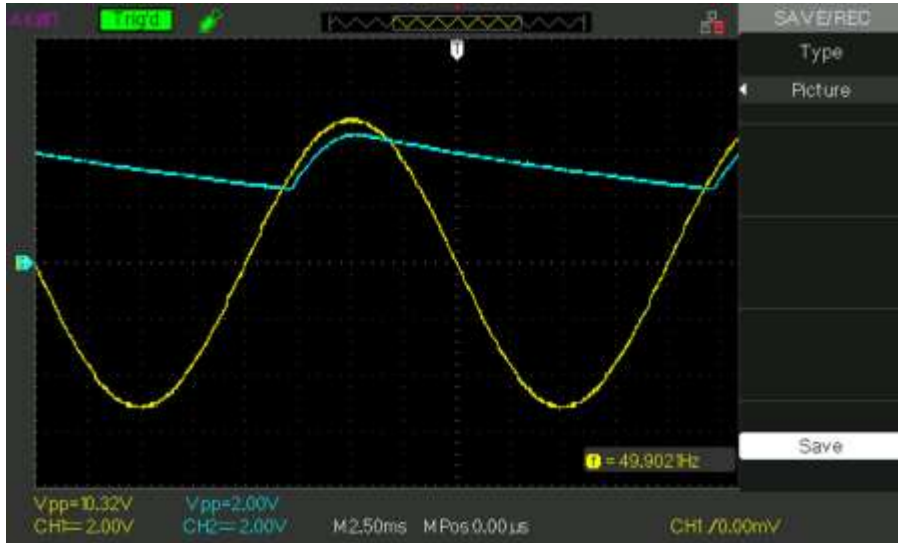


47uF

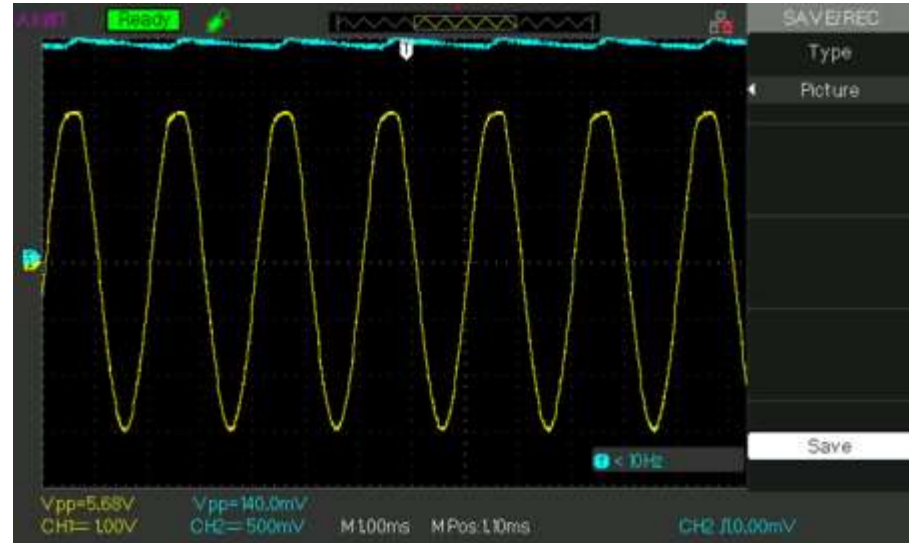

# Voltage amplifier

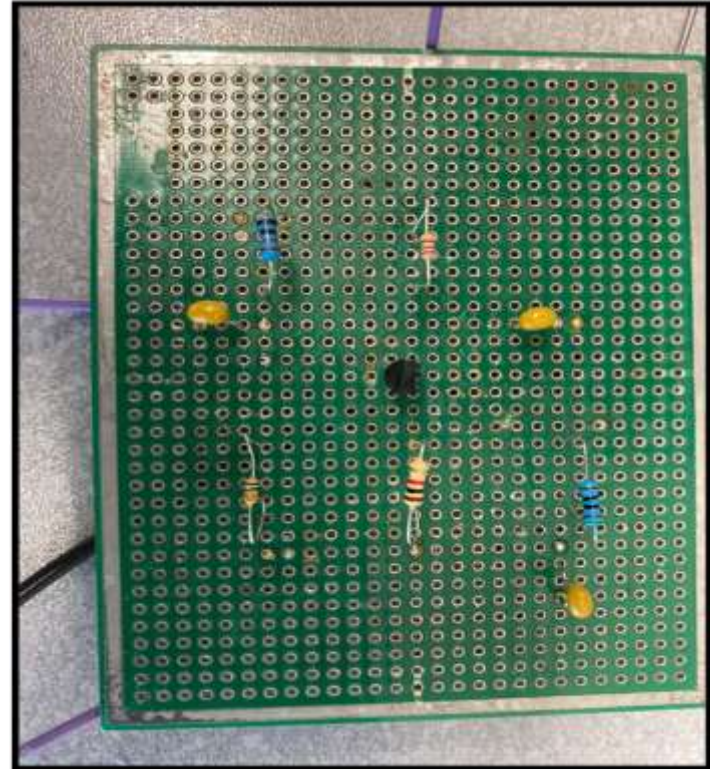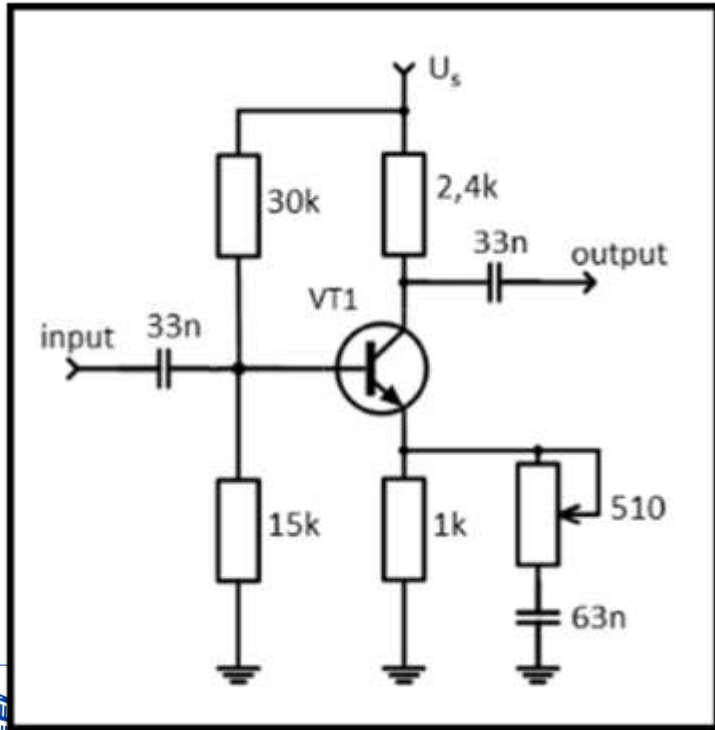

# Results cont'd: Amplifier

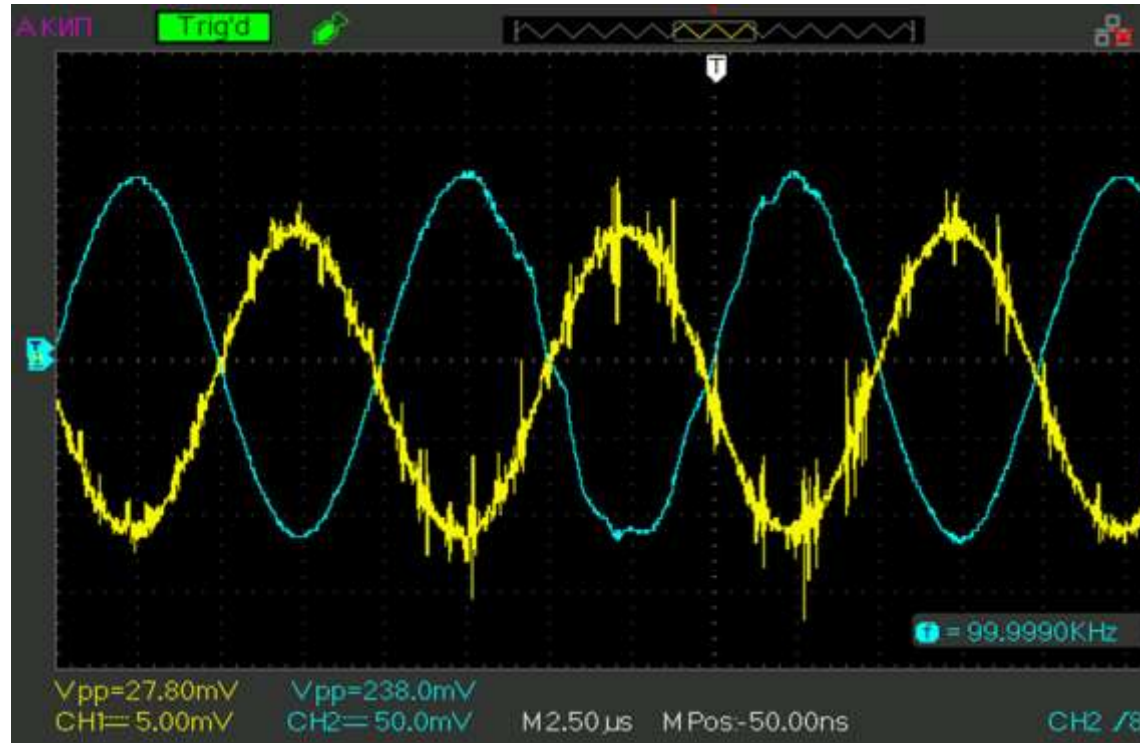

# Conclusions

- Waveguide has a higher wavelength as compared to coaxial and planar lines
- Matched loaded has an ideal SWR value approximately equal to 1
- The reactive dowel does a narrow band matching
- Diodes can assist channel the voltage direction in a circuit
- Increase in capacitance causes the AC behaviour to lean towards DC
- Transistors amplify the input signal power



