

Electronics and hand on training

Presented by:

Sara Said Abdelnour Abdelhak

Supervised by:

Dmitriy Belozerov

Introduction:

Almost every physicist-experiment requires particularly, engineer working with physical equipment who needs a basic understanding of electronics, e.g. for connection circuits and control elements design.




Description:

The practice is nominally divided into:



1- Basics part

2- Advanced part

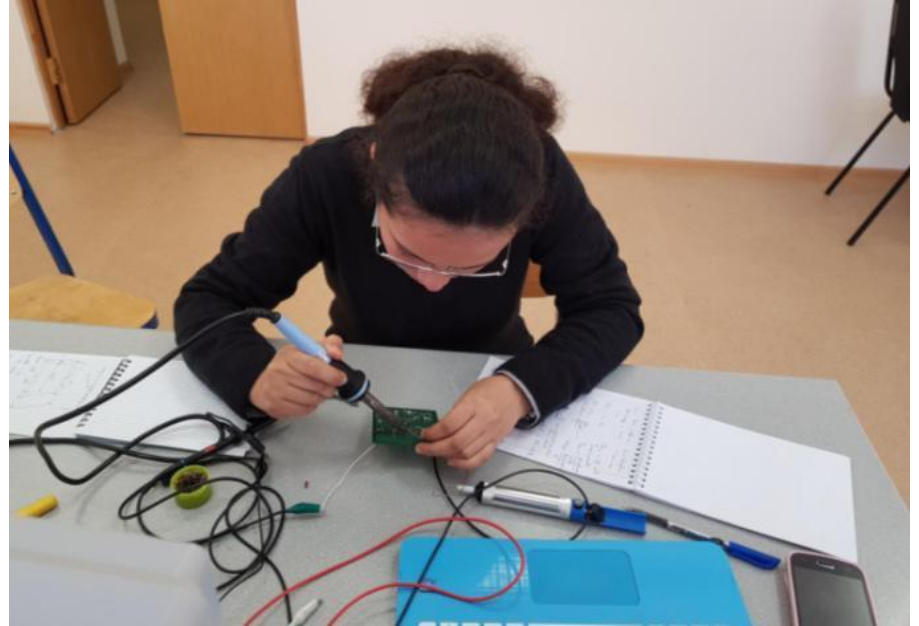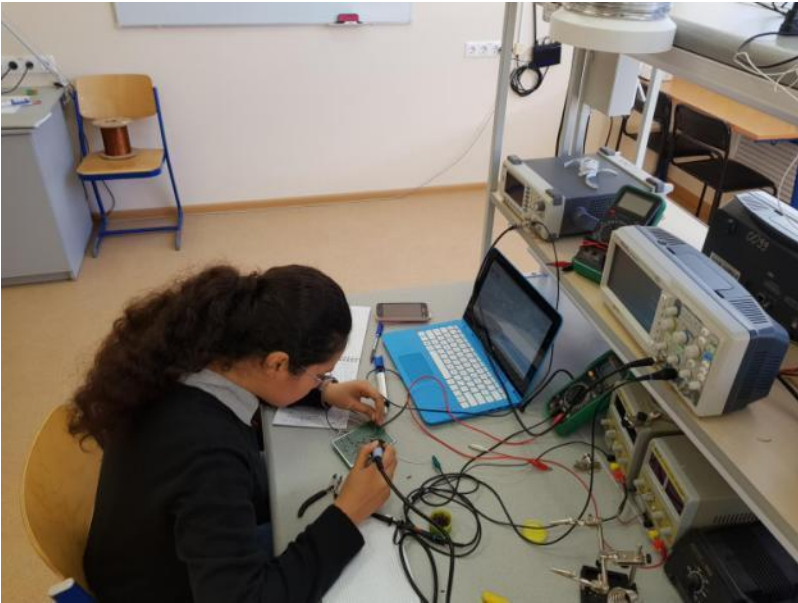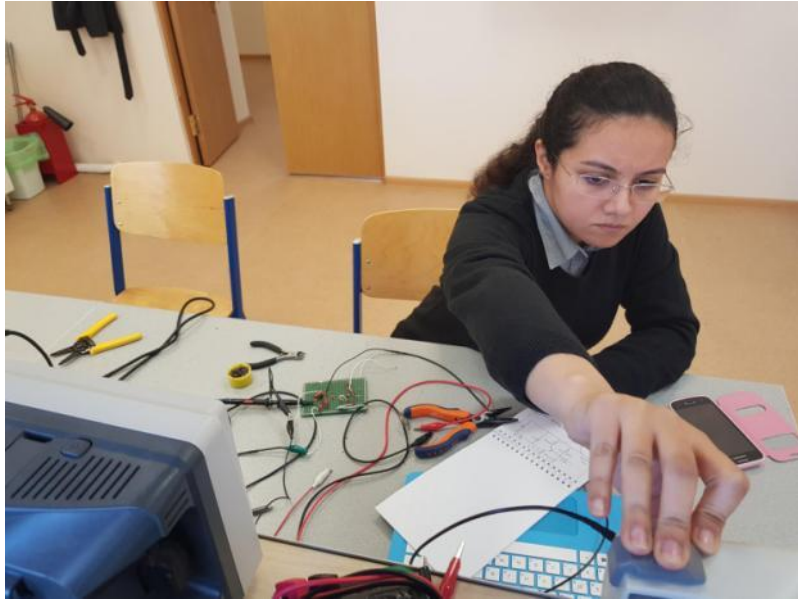
1-Basic (b) Part aims to acquire skills like



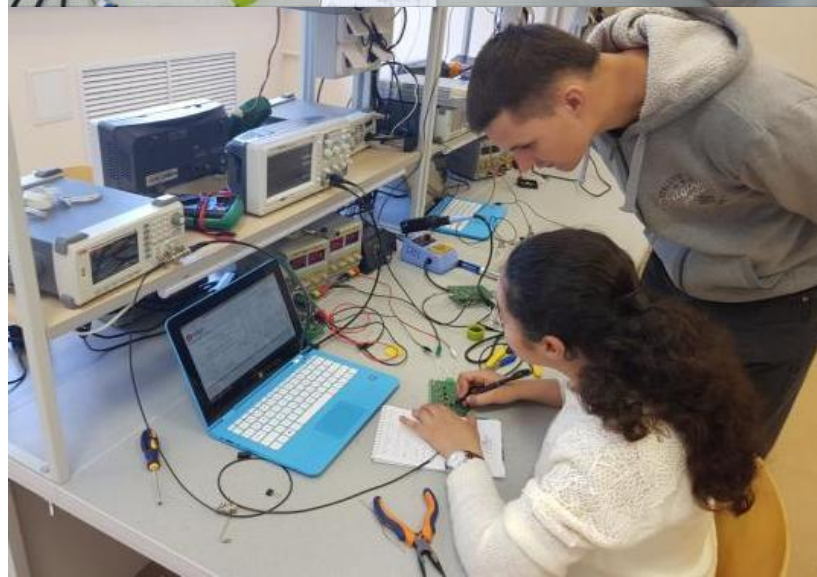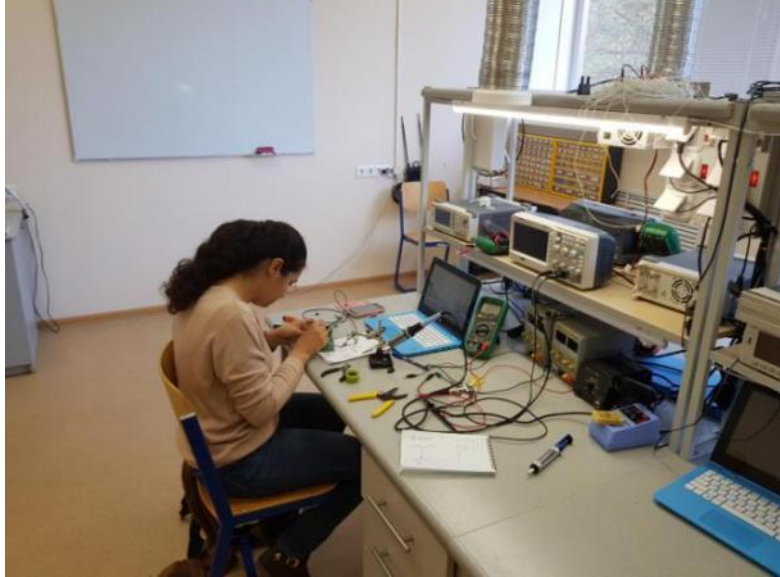2- Advanced (a) part: aims to calculate and assembling circuits used for coupling between instruments depending on specifications of experiments.



Cosmic rays

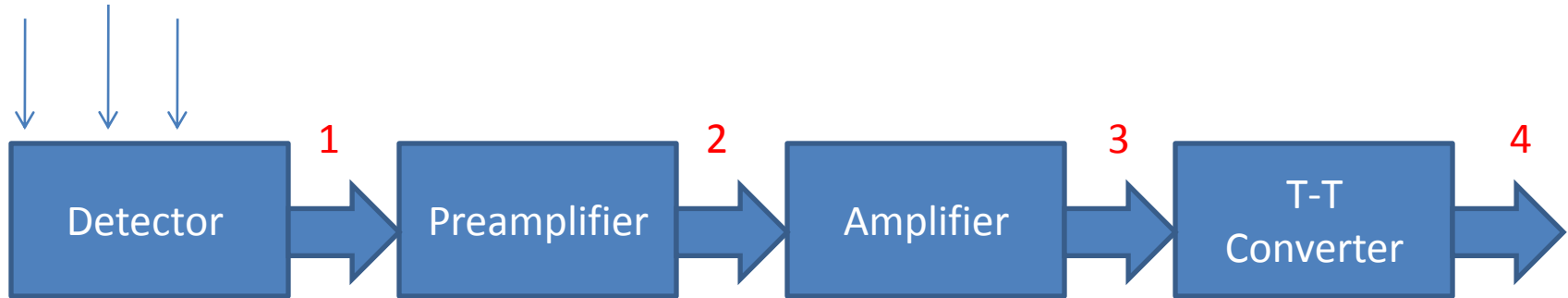


1-Signal with very low energy.

2-The same signal with higher power which is consistent to the next step.

3- Amplified signal with the same form and duration.


4- Signal with higher duration.

Preamplifier on CBC and CCC:

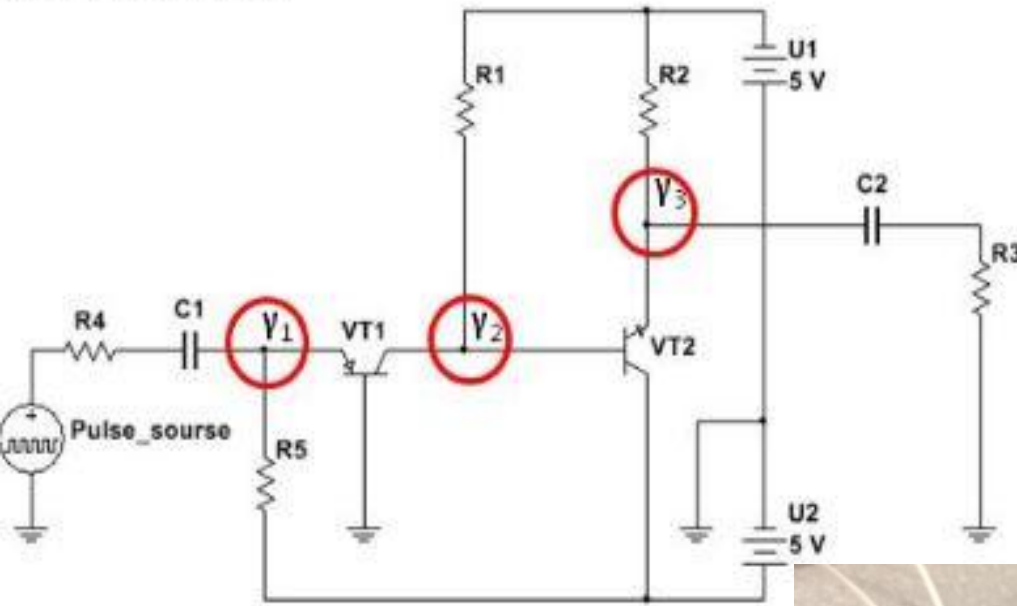


1- Adding voltage stabilizer to keep supply volt at 5V.

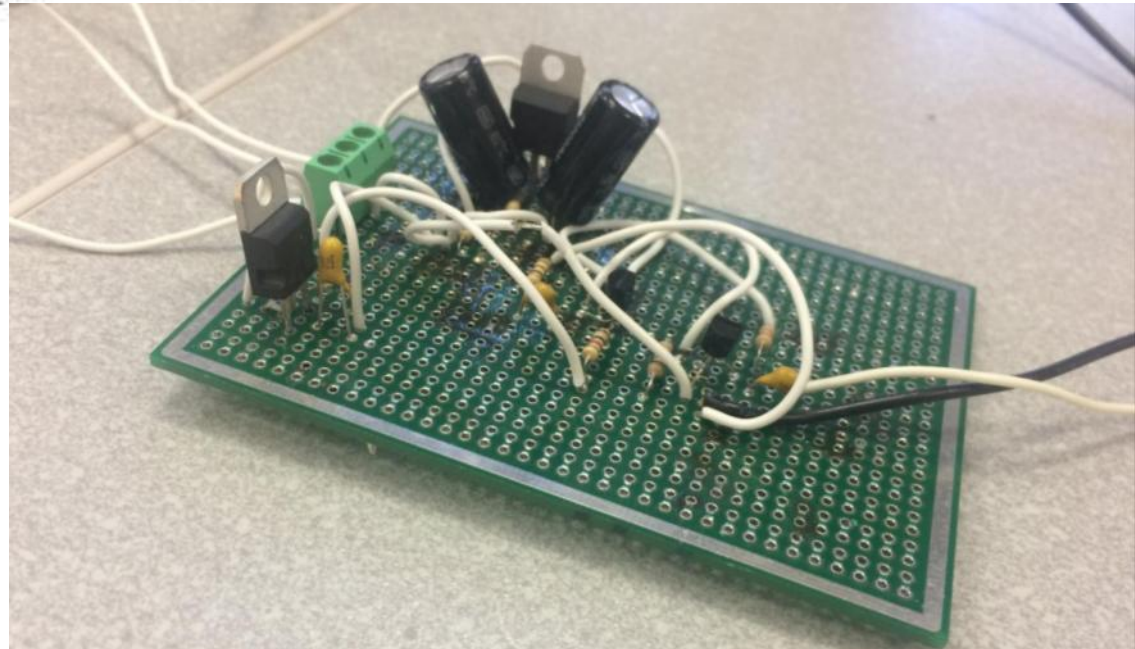2- Using LPF to cut noise from power supply.



Preamplifier on CBC and CCC:

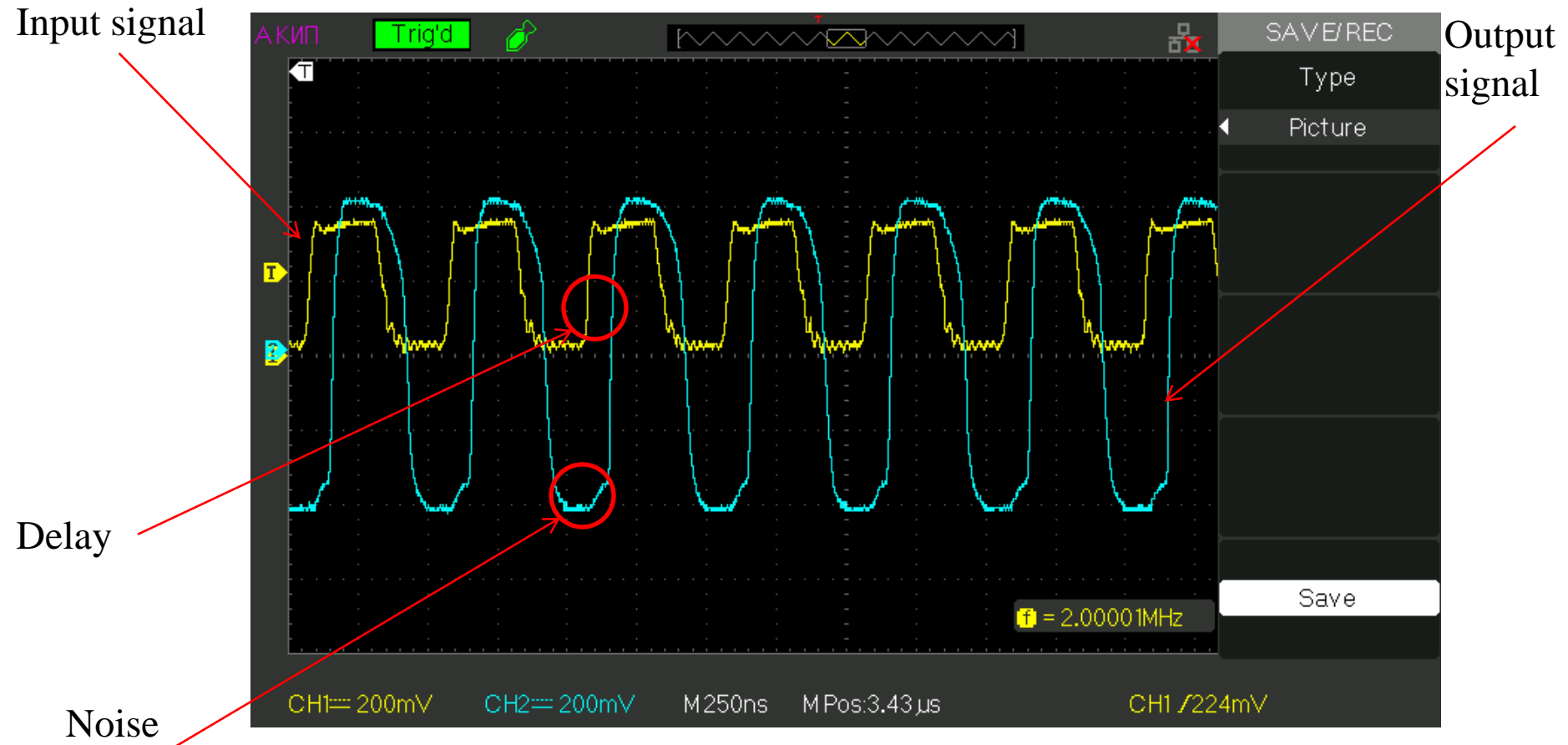1- Testing circuit using signal from wave generator




2- Signal from real cosmic ray detector


Positive distortion

High duration

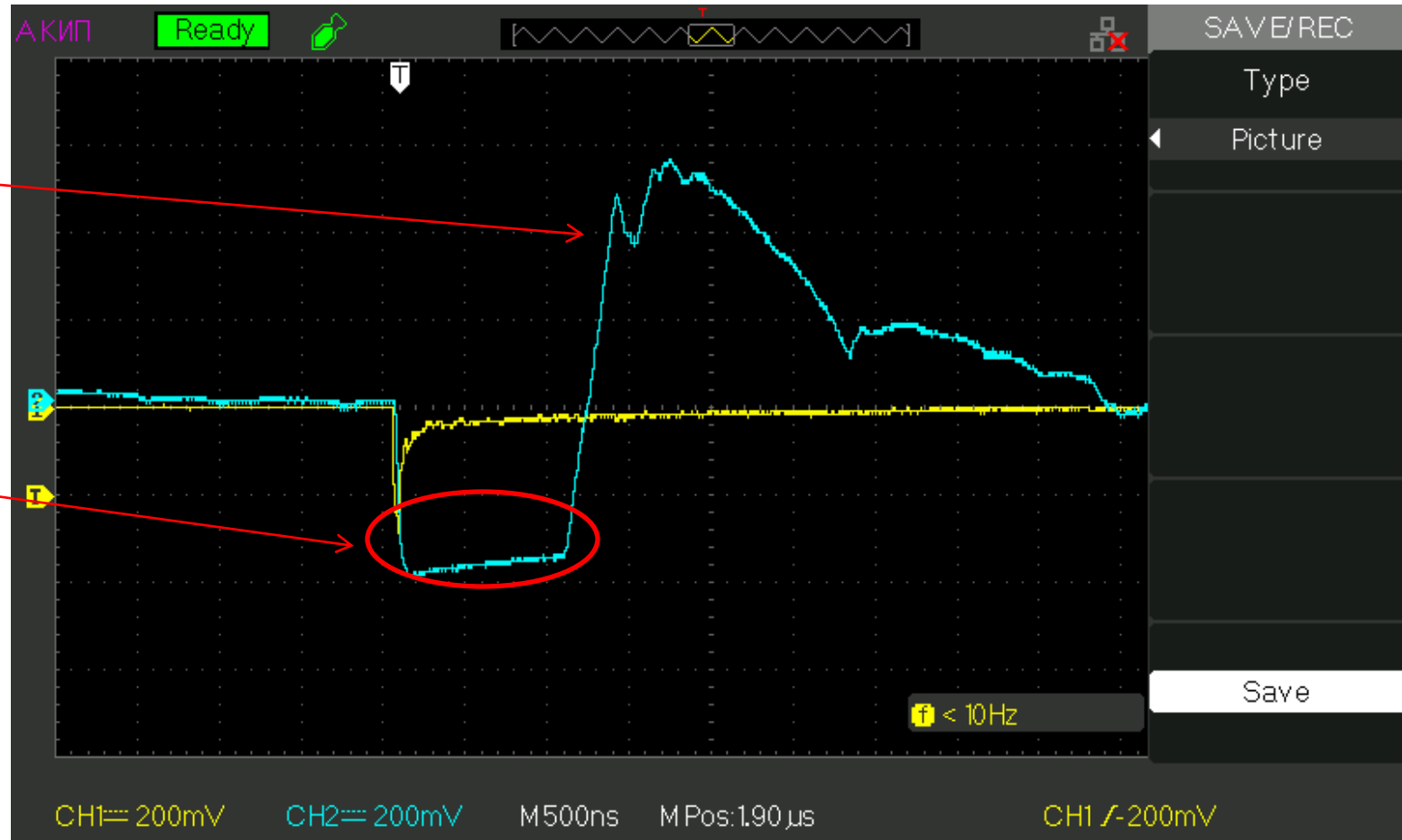$V_{in} = 300 \text{ mV}$
 $V_{out} = 400 \text{ mV}$
Gain = 1.33



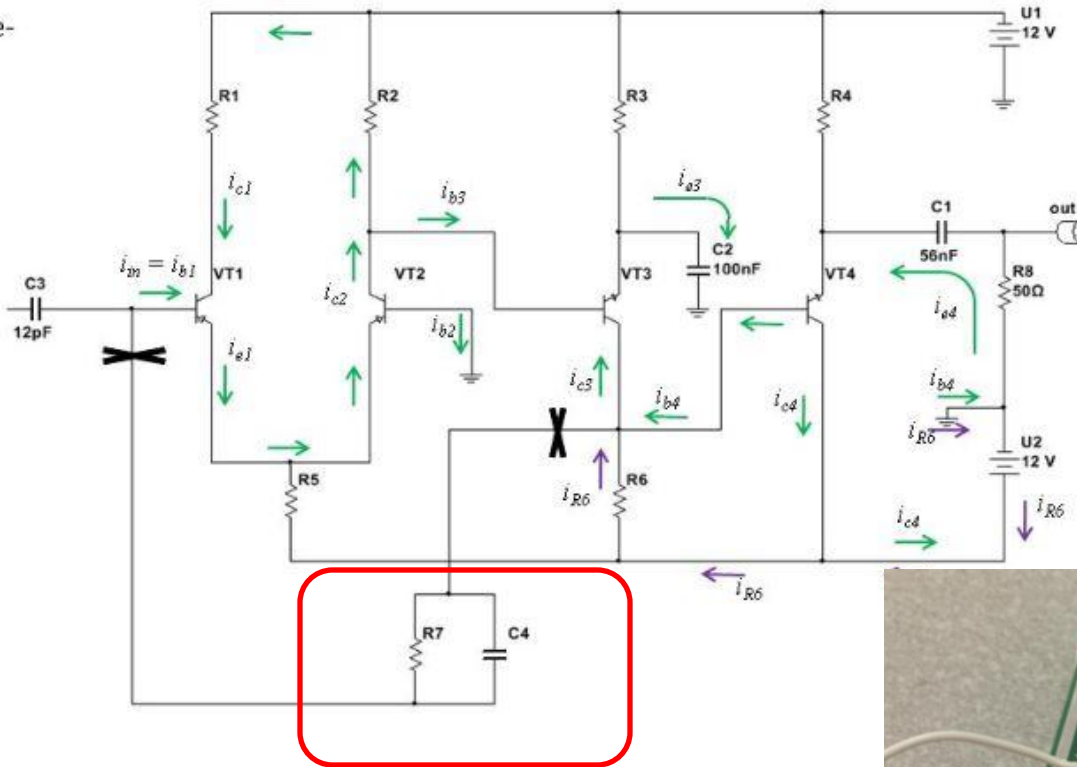
Charge-Sensitive amplifier based on DA, CE and CC.




1-O/P gain can be increased by increasing capacitance at input.

2-using LPF to cut noise from power supply.

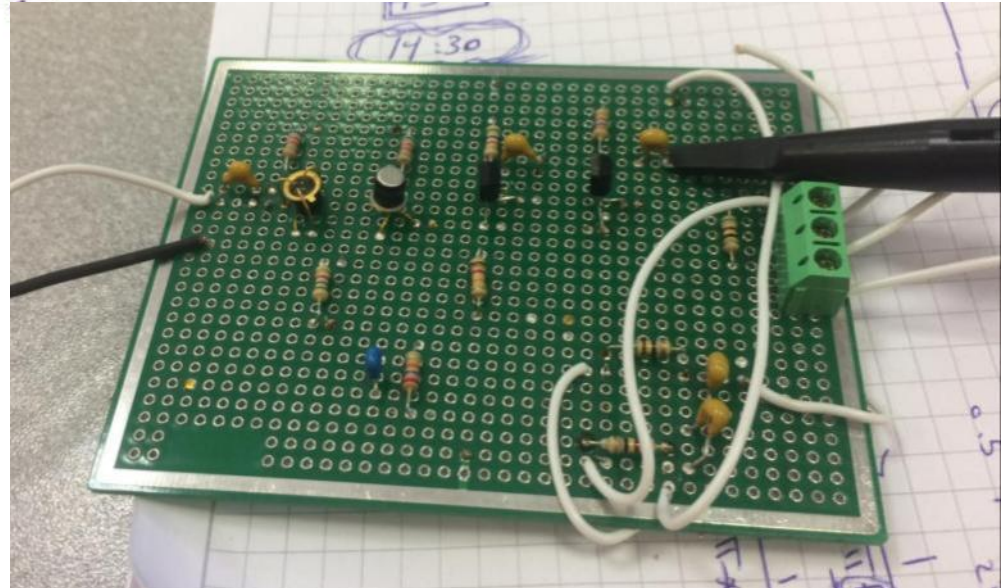
Tuning feed back circuit for input synchronization.



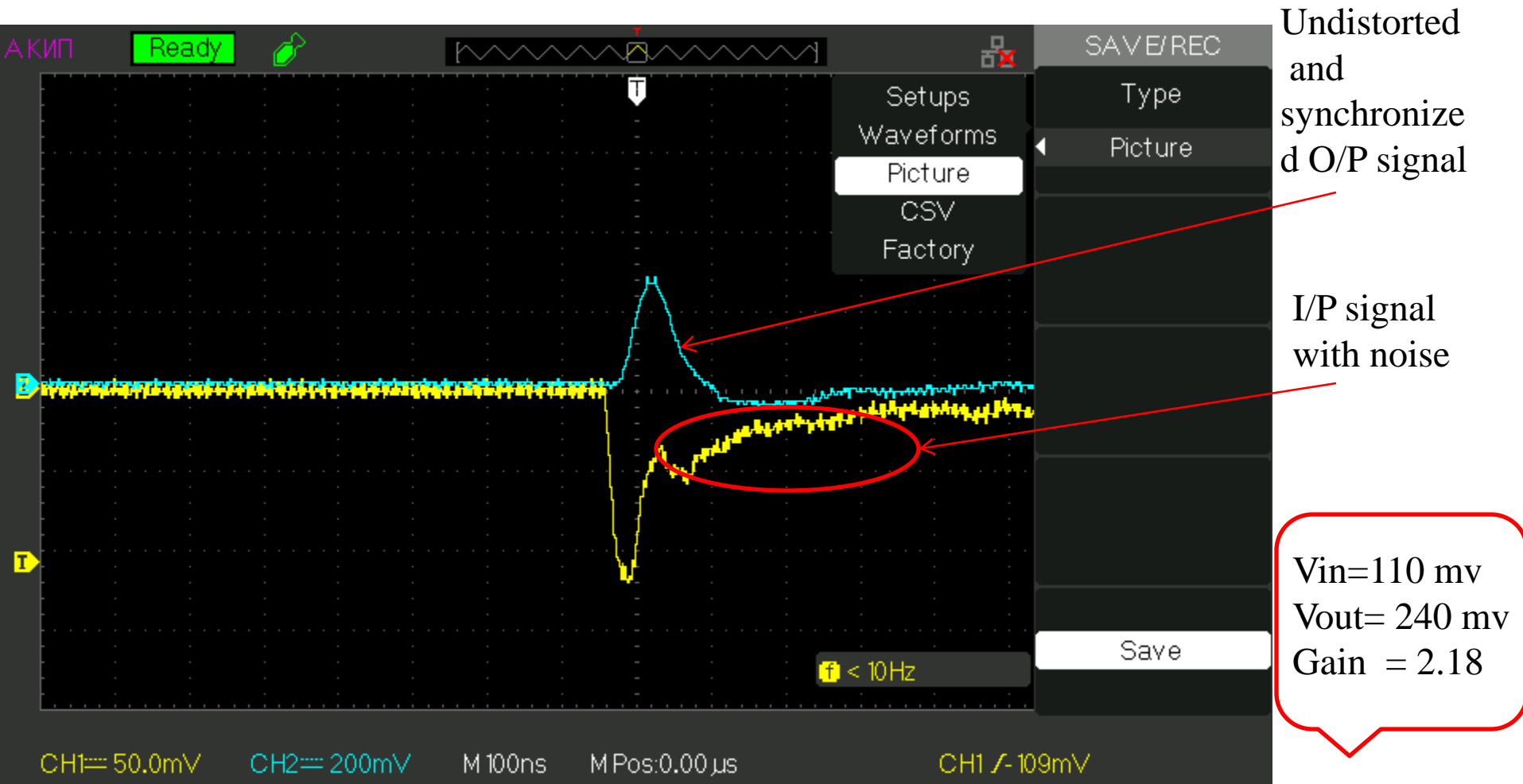Charge-Sensitive amplifier based on DA, CE and CC.




T-T Converter circuit:

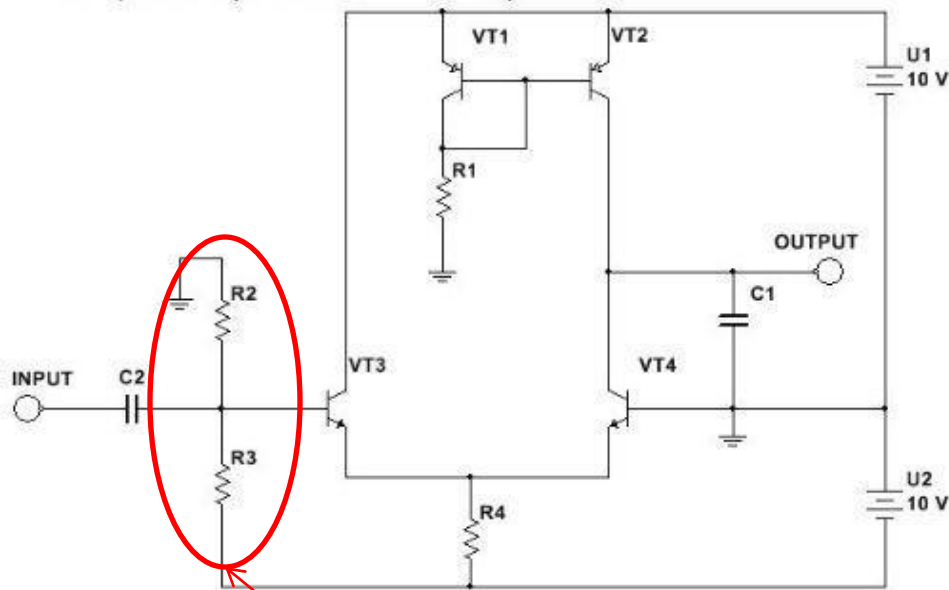


- 1- This circuit acts like a timer which keep the signal for long time.
- 2- Time gain can be increased by tuning R1 for charging time and (R1,R4) for discharging time.

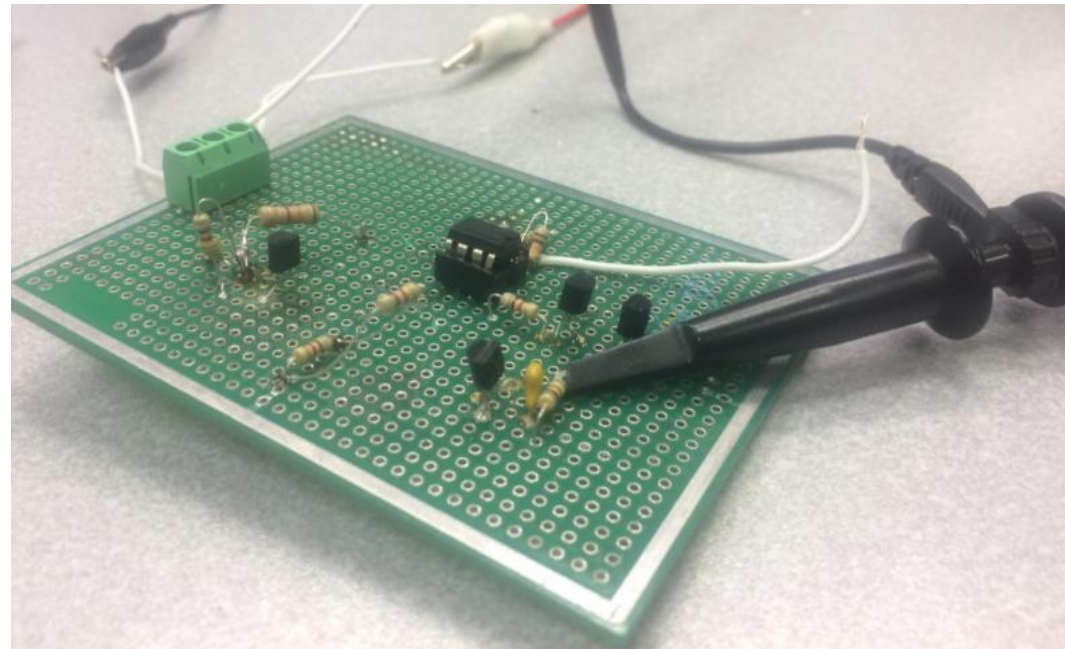
1-Voltage divider (R2 and R3) that set the threshold level of this circuit.



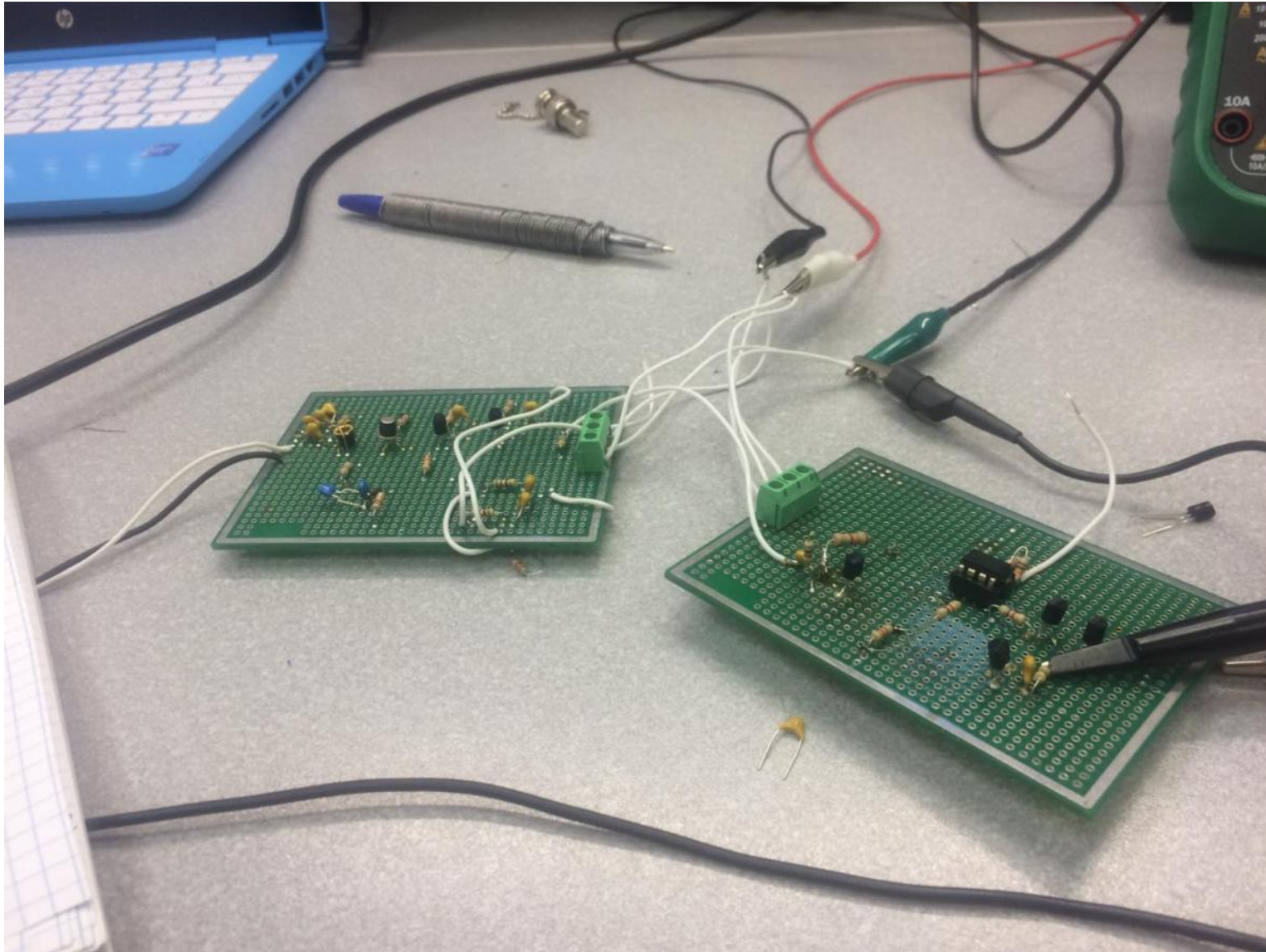Charge sensitive amplifier + T-T Converter




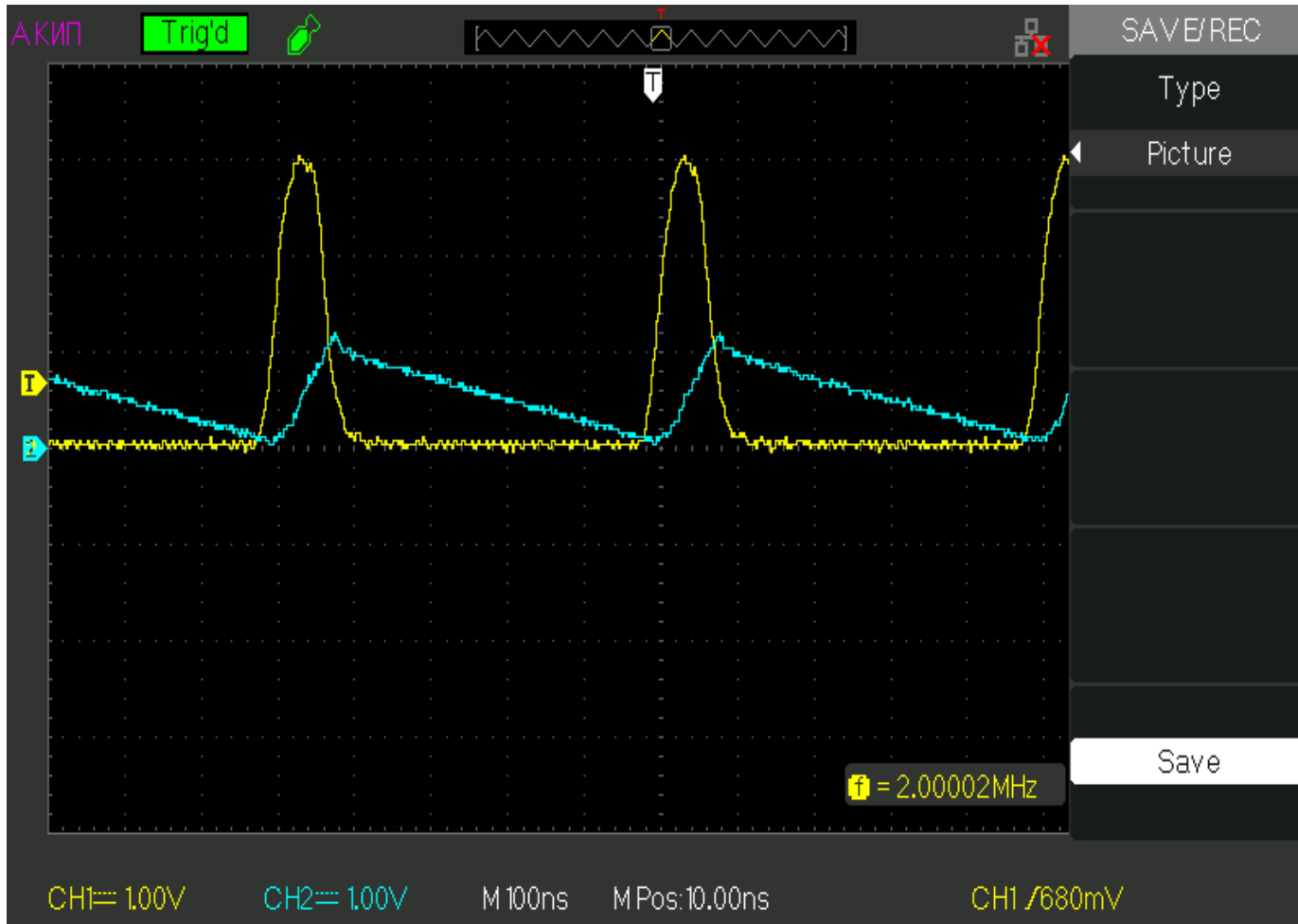4- Signal after time to time converter circuit



$T_{in} = 110 \text{ n sec}$
 $T_{out} = 500 \text{ n sec}$
Time gain 4.45

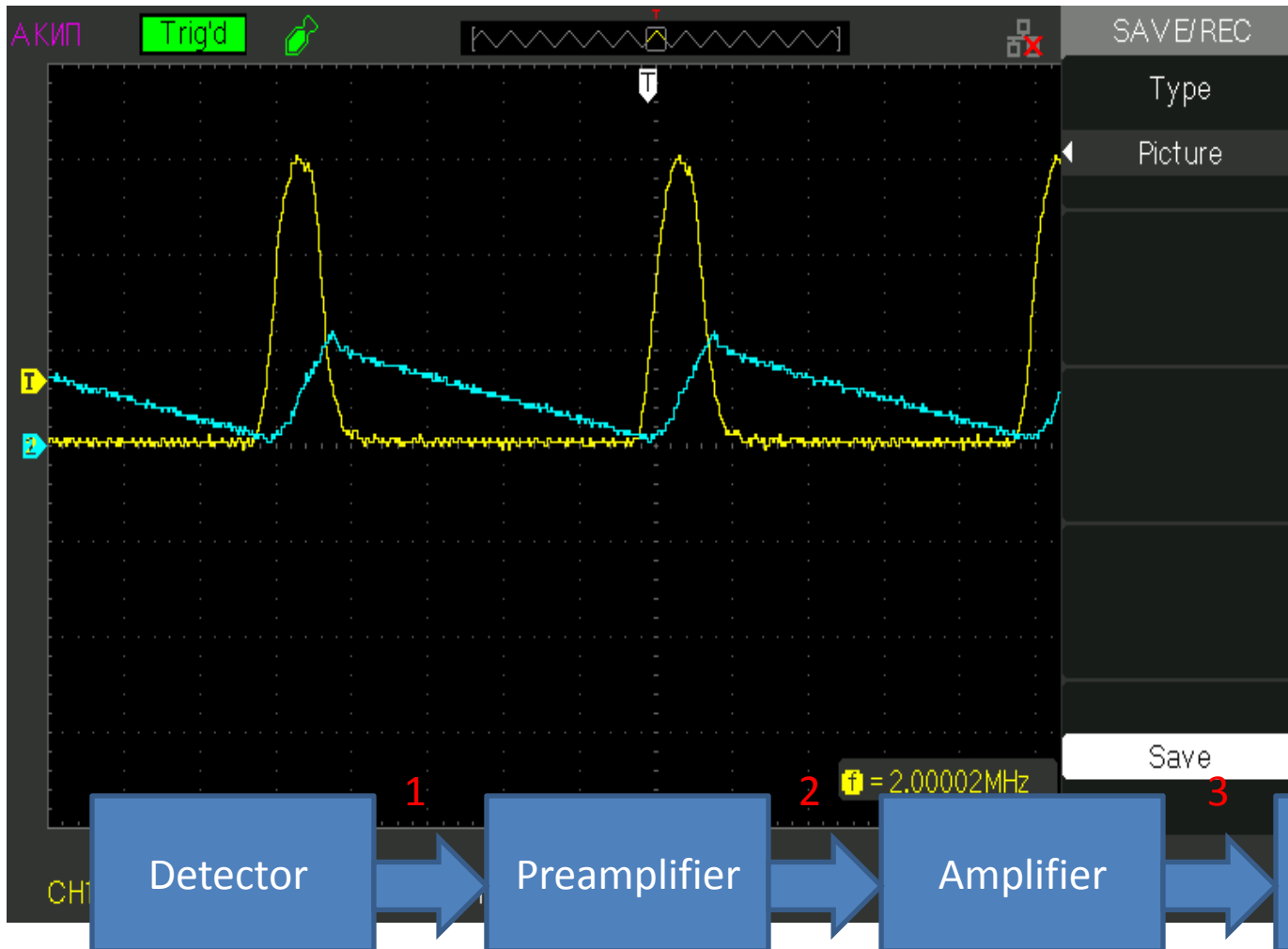4- Signal after time to time converter circuit



$T_{in} = 110 \text{ n sec}$
 $T_{out} = 500 \text{ n sec}$
Time gain 4.45

Conclusion:

1- Calculating and assembling different electronic circuits such as filters, preamplifiers and amplifiers.

2- Check the performance and sensitivity of different preamplifiers with different configurations.

3- Learn how to couple instruments for different scientific tasks.

*Thank
you*

